

**NANYANG  
TECHNOLOGICAL  
UNIVERSITY**

---

**SINGAPORE**

## **CE2004: Circuits & Signal Analysis - Lab Report (Lab 3)**

Do Anh Tu

Group SE2

S/N: B5

U1721947F

School of Computer Engineering

Nanyang Technological University, Singapore

15<sup>th</sup> November, 2018

## 1. Abstract

In Lab 3, we are asked to investigate the characteristics of linear op-amps circuits through their operation in some common applications, namely potentiometer, unity gain buffer, non-inverting amplifier, inverting amplifier and summing amplifier.

In this experiment, the standard industrial op-amp "741" is used in various circuit configurations to form the application discussed above. Figure 1 shows the pin-out diagram for the 741 op-amp that is referred to make connection for the circuits in experiments 2.1 and 2.2.

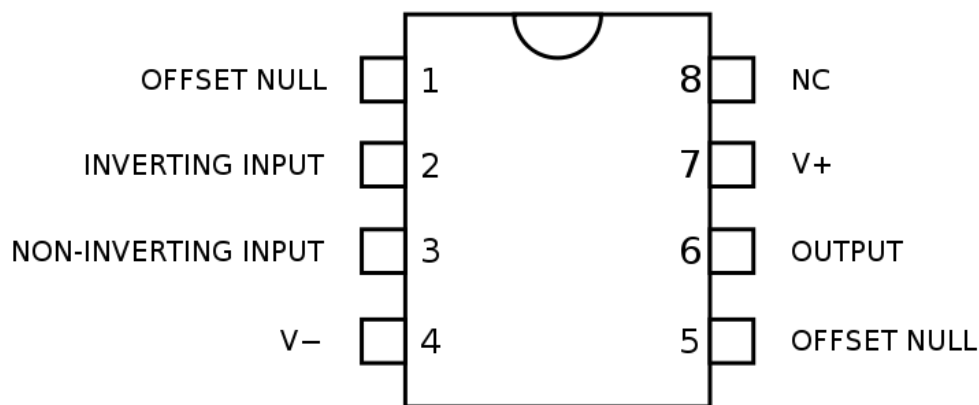


Figure 1. Pin-out diagram for "741" Op-amp

## 2. Experiments

### 2.1. Inverting Amplifier

#### a. Circuit Configuration with DC Power Supply as Input

The set up for Inverting Amplifier circuit with DC Power Supply is shown below in figure 2, where  $R_F = 33k\Omega$  or  $68k\Omega$  based on the lab manual.

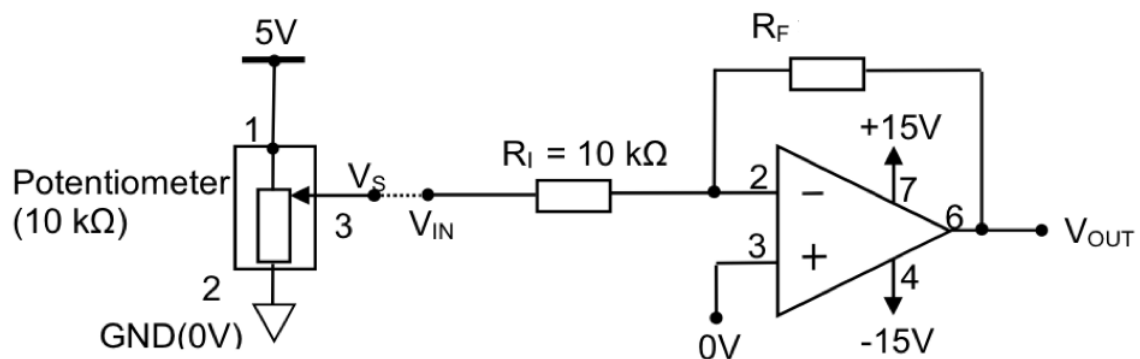


Figure 2. Inverting Amplifier Set-up (with DC Input,  $R_F = 33k\Omega$  or  $68k\Omega$ )

For inverting amplifiers, the gain of the amplifier  $A_0$  can be theoretically calculated as following (based on the set-up in figure 2):

$$A_0 = -\frac{R_f}{R_1} \quad (1)$$

From this calculated gain,  $V_{out}$  can be calculated by the formula:

$$V_{out} = A_0 * V_{in} \quad (2)$$

**Task 1: Measure  $V_{out}$ ,  $V_{in}$  for values of  $V_{in}$  from 0V to 5V in 1V intervals. Plot  $V_{out}$  against  $V_{in}$  to derive the voltage gain of inverting amplifier.**

We turn the potentiometer (knob) around to vary the  $V_{in}$  value. Using a Digital Multimeter to measure  $V_{out}$  and  $V_{in}$  at  $V_{in} = 0V, 1V, 2V, 3V, 4V, 5V$ .

**When  $R_f = 33k\Omega$ ,**

- From (1), **calculate voltage gain of the inverting op-amp =  $-33/10 = -3.3$**
- From (2),  $V_{out} = -3.3 * V_{in}$ . If after calculation  $V_{out} > 15V$ ,  $V_{out} = 15V$  and if  $V_{out} < -15V$ ,  $V_{out} = -15V$  (**theoretical saturation voltage is cap at +15V and -15V due to constraint of power supply**)
- The result of measurement for  $V_{out}$  at different interval of  $V_{in}$  as well as the corresponding calculated  $V_{out}$  is shown in table 1.

$V_{in}$	$V_{out}(\text{measured})$	$V_{out}(\text{calculated})$	Difference (absolute value)
0.000 V	0.002 V	0.000 V	0.002 V
1.001 V	-3.330 V	-3.303 V	0.027 V
2.000 V	-6.660 V	-6.600 V	0.060 V
3.002 V	-9.993 V	-9.907 V	0.086 V
4.000 V	-12.908 V	-13.200 V	0.292 V
5.004 V	-12.921 V	-15.000 V	2.079 V

Table 1.  $V_{out}$  measured vs theoretically calculated when  $R_f = 3.3k\Omega$

- Based on the  $V_{out}$  measured at the 6 intervals of  $V_{in}$ , we plot  $V_{out}$  against  $V_{in}$  and obtain a graph as shown in figure 3. Ignore the saturated portion of the graph for a best fit line to analyse actual voltage gain of the amplifier.
- From figure 3, take two points **(0.50, -1.64)** and **(2.50, -8.40)** which is in range where the op-amp output is not saturated yet. The gradient of the plot in this unsaturated range is  $\frac{-8.40 - (-1.64)}{2.50 - 0.50} = -3.38$ . Thus, **actual voltage gain of this inverting amplifier configuration = -3.38.**

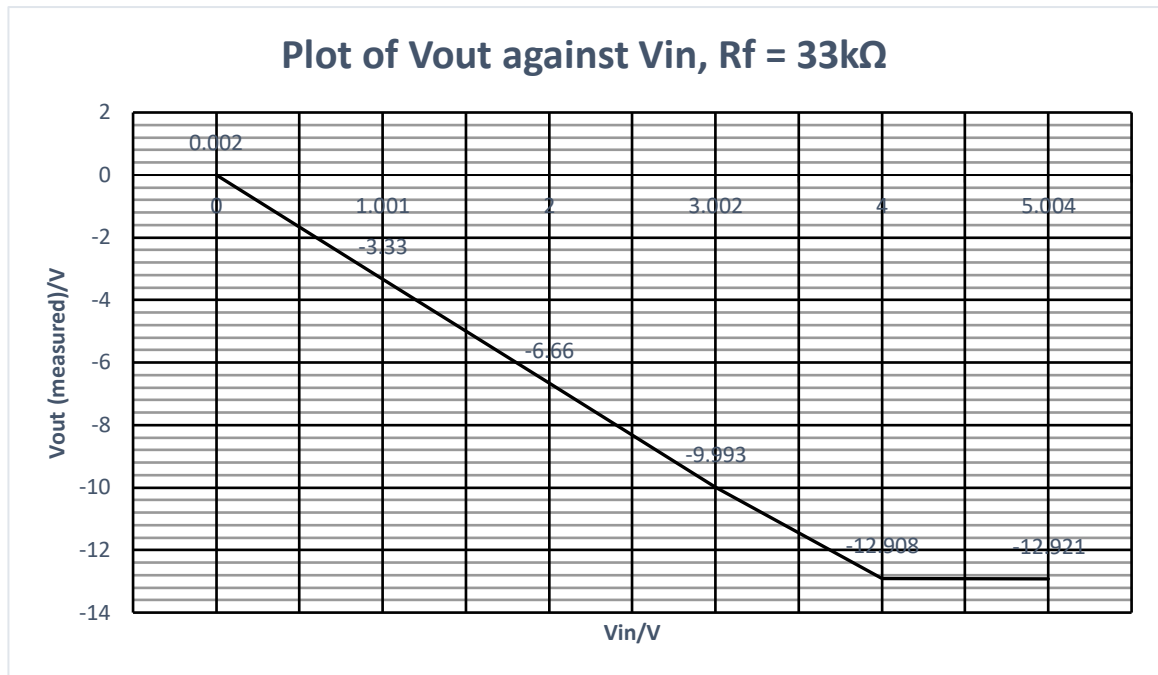


Figure 3. Plot of V<sub>out</sub> vs V<sub>in</sub> when R<sub>f</sub> = 33k $\Omega$

**When R<sub>f</sub> = 68k $\Omega$ ,**

- From (1), **calculate voltage gain of the inverting op-amp = -68/10 = -3.3**
- From (2), V<sub>out</sub> = -6.8 \* V<sub>in</sub>. If after calculation V<sub>out</sub> > 15V, V<sub>out</sub> = 15V and if V<sub>out</sub> < -15V, V<sub>out</sub> = -15V (as **theoretical saturation voltage is cap at +15V and -15V due to constraint of power supply**)
- The result of measurement for V<sub>out</sub> at different interval of V<sub>in</sub> as well as the corresponding calculated V<sub>out</sub> is shown in table 2.

V <sub>in</sub>	V <sub>out</sub> (measured)	V <sub>out</sub> (calculated)	Difference (absolute value)
0.000 V	0.002 V	0.000 V	0.002 V
1.002 V	-6.918 V	-6.815 V	0.103 V
2.004 V	-12.926 V	-13.627 V	0.701 V
3.003 V	-12.936 V	-15.000 V	2.064 V
4.000 V	-12.936 V	-15.000 V	2.064 V
5.002 V	-12.936 V	-15.000 V	2.064 V

Table 2. V<sub>out</sub> measured vs theoretically calculated when R<sub>f</sub> = 6.8k $\Omega$

- Based on the V<sub>out</sub> measured at the 6 intervals of V<sub>in</sub>, we plot V<sub>out</sub> against V<sub>in</sub> and obtain a graph as shown in figure 4. Ignore the saturated portion of the graph for a best fit line to analyse actual voltage gain of the amplifier.
- From figure 4, take two points **(0.50, -3.4)** and **(2.50, -9.96)** which is in range where the op-amp output is not saturated yet. The gradient of the plot in this unsaturated range is  $\frac{-10.0 - (-3.4)}{2.50 - 0.50} = -6.70$ . **Thus, actual voltage gain of this inverting amplifier configuration = -6.70.**

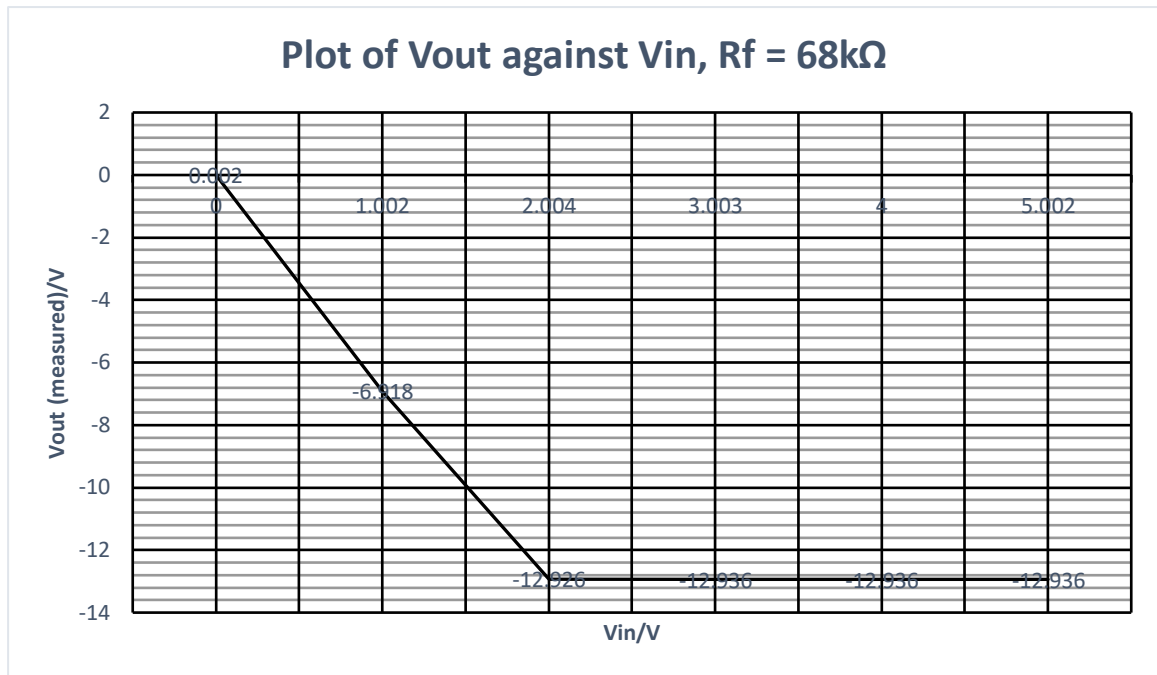


Figure 4. Plot of Vout vs Vin when Rf = 68kΩ

#### Observation:

- Actual voltage gains of both inverting amplifiers are **relatively close and consistent** with the theoretically predicted value and has **very high precision** (< 5.00% of error).
  - ✓ Rf = 33kΩ : actual gain = -3.38 vs calculated gain = -3.3. Percentage error =  $\frac{-3.38 - (-3.3)}{-3.3} * 100\% = 2.42\%$
  - ✓ Rf = 68kΩ : actual gain = -6.70 vs calculated gain = -6.8. Percentage error =  $\frac{-6.7 - (-6.8)}{-6.8} * 100\% = 1.47\%$
- The **voltage gains of both inverting amplifiers are negative**, the output voltages' polarity is in 180° phase difference with their input voltages. This is as expected from the theoretical derived voltage gains since we are using the inverting amplifiers in this task, which is known to produce an amplified output value with opposite polarity with input.
- The **saturated voltage for experimental op-amp is clipped at -12.936V** and is lower than the predicted clipped -15V by theory and based on the power supply given. This is because real, practical 741 op amps are non-ideal and is known to have output range of about 2V under the theoretical range (which is what observed in this case as  $|-15 + 12.936| = 2.064V$ )
- The **inverting amplifiers in our experiment behaves linearly** like expected (in non-saturated range). This is shown by the change in gradient between Rf = 33k and 68kΩ, where the later configuration result in a steeper gradient or decreases in Vout for the same Vin as the former. Thus a greater gain

magnitude produces a larger magnitude of change in  $V_{out}$  for the same interval of  $V_{in}$  like what being known for op-amps.

**Task 2: Set  $V_S$  to 2V. Disconnect the potentiometer output  $V_S$  from the amplifier  $V_{IN}$  and measure  $V_S$  again. Note any difference between the values measured.**

Refer to figure 2, we adjust the knob of potentiometer and measure the  $V_{in}$  value with multimeter such that it is = 2V (like the procedure to obtain  $V_{out}$  for corresponding interval of  $V_{in}$ ).

- **$V_S$  obtained when  $V_{in} = 2.000V$  is 2.5423V** instead of 2.000V as expected. For this inverting amplifier, the potential at inverting terminal is taken as a virtual ground ( $V_- = 0$ ) and is equal to  $V_+$  terminal value where it is connected to ground. In this configuration, the input impedance of amplifier is determined by  $R_1$ .
- Since  $R_1 = 10k\Omega$  and is finite, there is current flowing into the  $V_-$  terminal =  $(V_S - V_-)/R_1 = (2.5423 - 0)/10k = 2.5423 \text{ mA}$ . Therefore, **the input impedance is not ideal (infinite)** in this inverting op-amp as  $Z_{in} = R_1 = V_S/I = 2.5423/2.5423m = 10k\Omega$ . As the input impedance is finite, **there is current flowing from the power supply (potentiometer where  $V_S$ )**. Thus, the actual  $V_{in}$  received by amplifier is less than  $V_S$  ( $2.000V < 2.5423V$ ) due to the input impedance value, which induce a small current flowing into the  $V_-$  terminal and **lead to voltage drop across  $R_1$** , explained the mis-match of  $V_S$  value.

#### b. Circuit Configuration with Sinusoidal Signal as Input

**Task 3: Set  $R_F = 33k\Omega$ . Connect  $V_{IN}$  to the output of a function generator. Connect the -ve terminal of the function generator to GND of the power supply (not to -15V). Set the function generator to supply a 1KHz sine wave of  $3V_{PK-PK}$  amplitude. Observe the waveforms at  $V_{IN}$  and  $V_{OUT}$  on the oscilloscope and sketch the waveforms.**

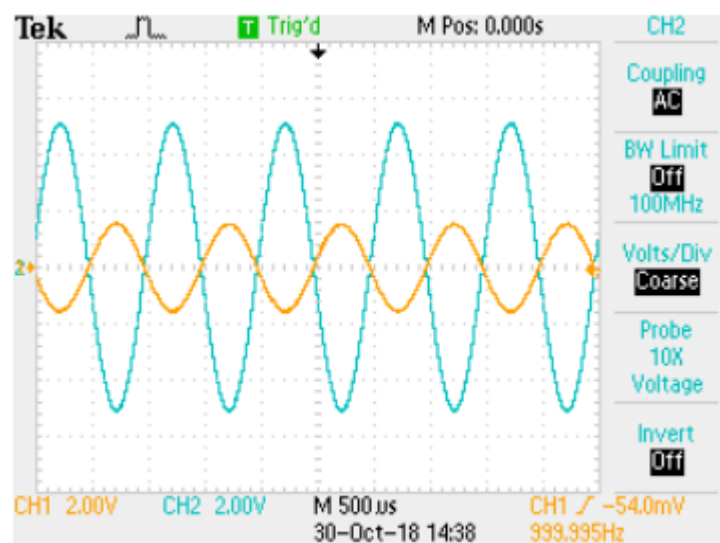


Figure 5. Waveform of  $V_{out}$  (blue) vs  $V_{in}$  (yellow) for inverting amplifier with  $R_f=33k\Omega$

Following the procedure described above, make the change to figure 2 circuit configuration. We can obtain the waveform as shown in figure 5 from oscilloscope.

- **$V_{out}$  waveform obtained is a complete sinusoidal waveform.** This shown that there were no clipping phenomenon happens and the  $V_{out}$  due to  $V_{in}$  waveform was not at saturated value at all. This is as expected as the experimental gain was determined to be -3.38 for this amplifier and  $V_{in} = 3V$  (Peak-Peak from -1.5V to 1.5V, offset = 0 ). Thus the max  $V_{out} = 5.07V$  and min  $V_{out} = -5.07V$ , which is way lower than the saturated value of 12.936V and -12.936V determined above.
- Polarity wise, **the  $V_{out}$  waveform is  $180^\circ$  out of phase with the  $V_{in}$  waveform.** This is the expected behaviour for an inverting amplifier with a negative gain.
- Amplitude wise, **the  $V_{out}$  waveform's amplitude is 3.38 times the  $V_{in}$  amplitude** (consistently throughout the waveform). This is because the gain of this amplifier configuration has magnitude  $> 1$  so the amplitude change should be more than unity, equal to the magnitude of voltage gain =  $|-3.38| = 3.38$  as determined.
- **The waveform of input and output is continuous and  $V_{out}$  change linearly with  $V_{in}$  value**, shown by the corresponding sinusoidal waveform correspond to that of  $V_{in}$ .

## 2.2. Non-Inverting Amplifier

### a. Circuit Configuration with DC Power Supply as Input

The set up for Non-Inverting Amplifier circuit with DC Power Supply is shown below in figure 6 based on the lab manual.

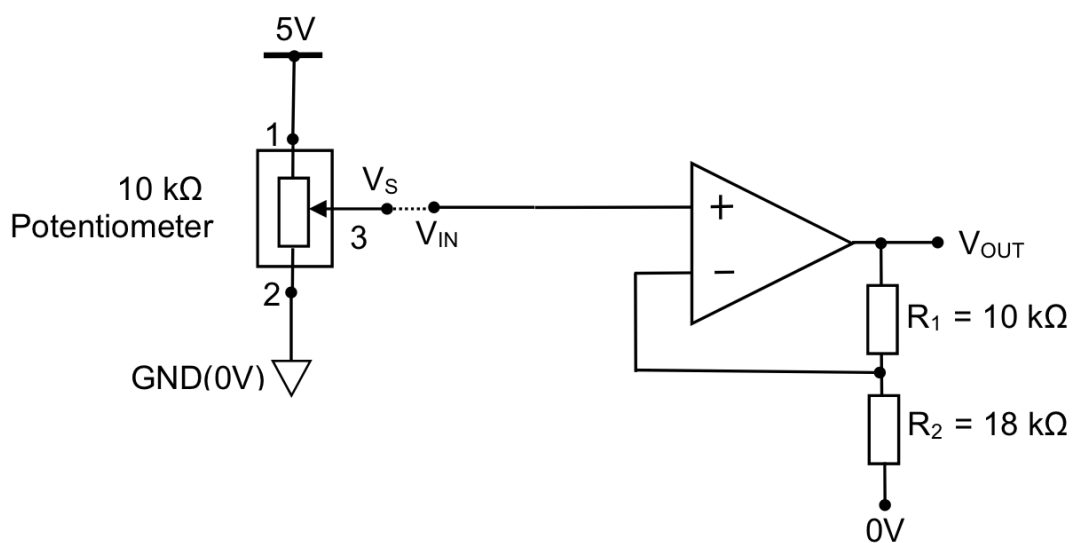


Figure 6. Non-Inverting Amplifier Set-up (with DC Input)

For non-inverting amplifiers, the gain of the amplifier  $A_0$  can be theoretically calculated as following (based on the set-up in figure 2):

$$A_0 = 1 + \frac{R_1}{R_2} \quad (3)$$

From this calculated gain,  $V_{out}$  can be calculated by the formula:

$$V_{out} = A_0 * V_{in} \quad (4)$$

**Task 1: Measure  $V_{out}$ ,  $V_{in}$  for values of  $V_{in}$  from 0V to 5V in 1V intervals. Plot  $V_{out}$  against  $V_{in}$  to derive the voltage gain of non-inverting amplifier.**

We turn the potentiometer (knob) around to vary the  $V_{in}$  value. Using a Digital Multimeter to measure  $V_{out}$  and  $V_{in}$  at  $V_{in} = 0V, 1V, 2V, 3V, 4V, 5V$ .

- From (3), **calculate voltage gain of the non-inverting op-amp =  $1 + (10/18) = 1.56$**
- From (4),  $V_{out} = 1.556 * V_{in}$ . If after calculation  $V_{out} > 15V$ ,  $V_{out} = 15V$  and if  $V_{out} < -15V$ ,  $V_{out} = -15V$  (**theoretical saturation voltage is cap at +15V and -15V due to constraint of power supply**)
- The result of measurement for  $V_{out}$  at different interval of  $V_{in}$  as well as the corresponding calculated  $V_{out}$  is shown in table 3.

$V_{in}$	$V_{out}(\text{measured})$	$V_{out}(\text{calculated})$	Difference (absolute value)
0.000 V	0.001 V	0.000 V	0.001 V
1.000 V	1.555 V	1.556 V	0.001 V
2.002 V	3.112 V	3.115 V	0.003 V
3.001 V	4.664 V	4.670 V	0.006 V
4.000 V	6.215 V	6.224 V	0.009 V
5.000 V	7.768 V	7.780 V	0.012 V

Table 3.  $V_{out}$  measured vs theoretically calculated for non-inverting amplifier

- Based on the  $V_{out}$  measured at the 6 intervals of  $V_{in}$ , we plot  $V_{out}$  against  $V_{in}$  and obtain a graph as shown in figure 7. This is also the best fit line.
- From figure 7, take two points **(0.50, 0.80)** and **(4.50, 7.00)** which is in range where the op-amp output is not saturated yet. The gradient of the plot in this unsaturated range is  $\frac{7.00-0.80}{4.50-0.50} = 1.55$ . **Thus, actual voltage gain of this non-inverting amplifier configuration = 1.55.**

#### Observations:

- **Actual voltage gain of non-inverting amplifier is relatively close and consistent** with the theoretically predicted value and has very **high precision** (< 5.00% of error). Actual gain = 1.55 vs calculated gain = 1.556. Percentage error =  $\frac{1.556-1.55}{1.556} * 100\% = 0.39\%$



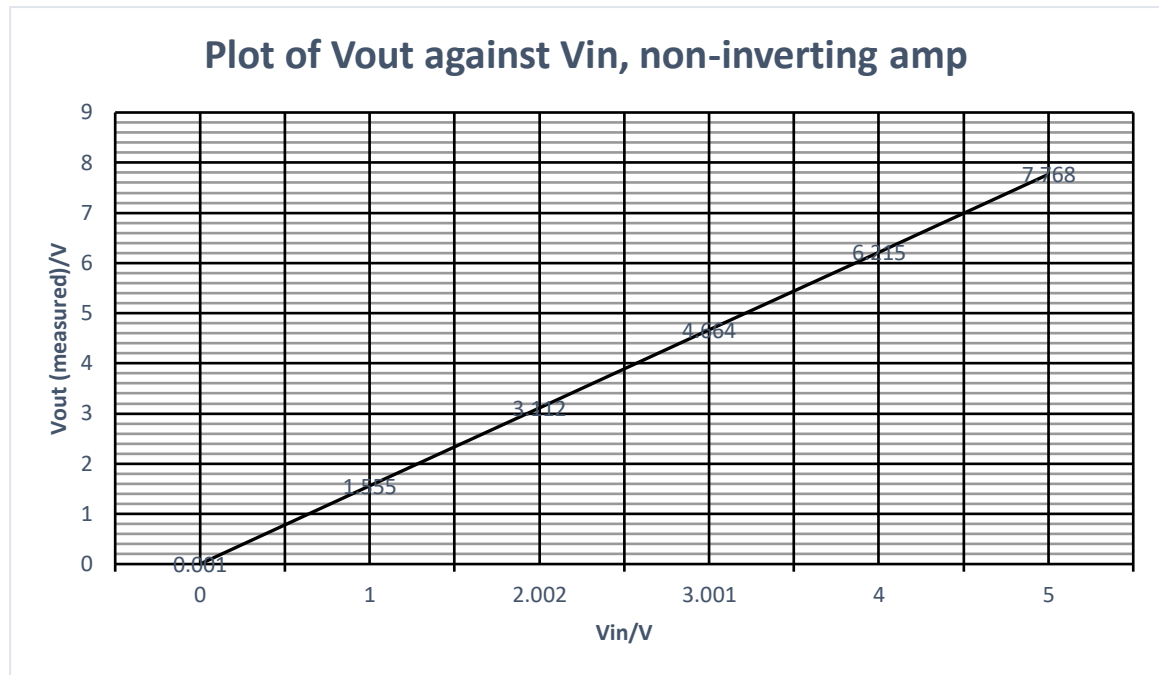


Figure 7. Plot of  $V_{out}$  against  $V_{in}$ , non-inverting amp

- The **voltage gain of non-inverting amplifier is non-negative**, the output voltages' polarity is in phase with input voltages. This is as expected from the theoretical derived voltage gain since we are using the non-inverting amplifier in this task, which is known to produce an amplified output value with no change in polarity compared to input.
- **No saturation range in output** as max  $V_{out}$  recorded = 7.768V and is way lower than the saturated voltage level determined in part 2.1.a
- **The non-inverting amplifiers in our experiment behaves linearly** like expected. At every input interval, the output voltage is amplified by a gain factor of 1.55 as determined above. The gradient of the plot is a nice linear model, with very big linear region (no sharp swing of value of output voltage from 0 to saturated value).

**Task 2: Set  $V_S$  to 2V. Disconnect the potentiometer output  $V_S$  from the amplifier  $V_{IN}$  and measure  $V_S$  again. Note any difference between the values measured.**

Refer to figure 6, we adjust the knob of potentiometer and measure the  $V_{in}$  value with multimeter such that it is = 2V (similar to the procedure to obtain  $V_{out}$  for corresponding interval of  $V_{in}$ ).

- **$V_S$  obtained when  $V_{in} = 2.000V$  is 2.000V** as expected. For this non-inverting amplifier, the potential at both inverting and non-inverting terminal is assumed to be equal.
- Unlike in 2.1.a, where the amplifier has  $R_1 = 10k\Omega$ , this non-inverting amplifier do not have this input resistor. Thus, the input impedance can be assumed to be infinite and as a result, no current flow into the non-inverting terminal. Therefore, **there is no current flowing from the power supply (potentiometer where  $V_S$ ) into  $V_+$  (non-inverting terminal)**. Thus, the actual

$V_{in}$  is equal to  $V_s$ . Due to the input impedance value = infinite, **no voltage drops between  $V_s$  into  $V_+$  terminal**, explained the expected of  $V_s$  value to be the same with or without connecting to the amplifier.

#### b. Circuit Configuration with Sinusoidal Signal as Input

**Task 3: Connect  $V_{in}$  to the output of a function generator. Connect the -ve terminal of the function generator to GND of the power supply (not to -15V). Set the function generator to supply a 1KHz sine wave of  $3V_{PK-PK}$  amplitude. Observe the waveforms at  $V_{in}$  and  $V_{out}$  on the oscilloscope and sketch the waveforms.**

Following the procedure described above, make the change to figure 6 circuit configuration. We can obtain the waveform as shown in figure 8 from oscilloscope.

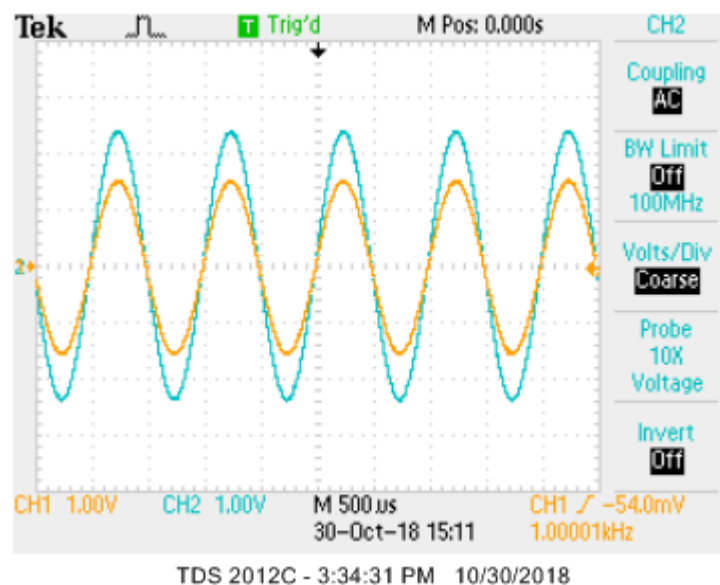


Figure 8 Waveform of  $V_{out}$  (blue) vs  $V_{in}$  (yellow) for non-inverting amplifier

- **$V_{out}$  waveform obtained is a complete sinusoidal waveform.** This shown that there were no clipping phenomenon happens and the  $V_{out}$  due to  $V_{in}$  waveform was not at saturated value at all. This is as expected as the experimental gain was determined to be 1.55 for this amplifier and  $V_{in} = 3V$  (Peak-Peak from -1.5V to 1.5V, offset = 0 ). Thus the max  $V_{out} = 2.325V$  and min  $V_{out} = -2.325V$ , which is way lower than the saturated value of 12.936V and -12.936V determined above in 2.1.a.
- Polarity wise, **the  $V_{out}$  waveform is in phase with the  $V_{in}$  waveform.** This is the expected behaviour for an non-inverting amplifier with a positive gain.
- Amplitude wise, **the  $V_{out}$  waveform's amplitude is 1.55 times the  $V_{in}$  amplitude** (consistently throughout the waveform). This is because the gain of this amplifier configuration has magnitude  $> 1$  so the amplitude change should be more than unity, equal to the magnitude of voltage gain = 1.55 as determined.

- The waveform of input and output is continuous and  $V_{out}$  change linearly with  $V_{in}$  value, shown by the corresponding sinusoidal waveform correspond to that of  $V_{in}$ .

### 2.3. Unity Gain Amplifier

#### a. Circuit Configuration with DC Power Supply as Input

The set up for Unity Gain Amplifier circuit with DC Power Supply is shown below in figure 9 based on the lab manual.

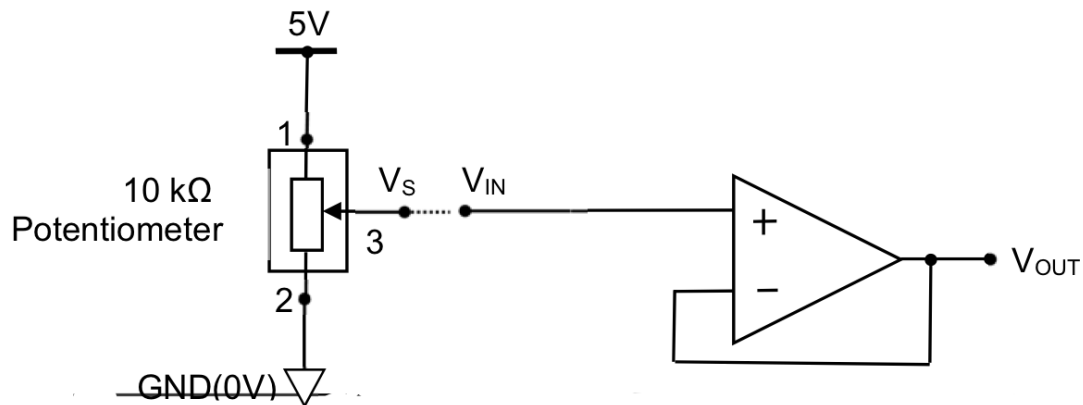


Figure 9 Unity Gain Amplifier Set-up (with DC Input)

**Task 1: Measure  $V_{out}$ ,  $V_{in}$  for values of  $V_{in}$  from 0V to 5V in 1V intervals. Plot  $V_{out}$  against  $V_{in}$  to derive the voltage gain of Unity Gain amplifier.**

As Unity Gain Amplifier is basically a non-inverting amplifier with short circuit in place of  $R_1$ . We can reuse the formula (3) and (4) described in 2.2.a.

We turn the potentiometer (knob) around to vary the  $V_{in}$  value. Using a Digital Multimeter to measure  $V_{out}$  and  $V_{in}$  at  $V_{in} = 0V, 1V, 2V, 3V, 4V, 5V$ .

- From (3), calculate voltage gain of the unity gain amplifier =  $1 + (0/18) = 1$  (as s/c means resistance = 0)
- From (4),  $V_{out} = V_{in}$ . If after calculation  $V_{out} > 15V$ ,  $V_{out} = 15V$  and if  $V_{out} < -15V$ ,  $V_{out} = -15V$  (theoretical saturation voltage is cap at +15V and -15V due to constraint of power supply)
- The result of measurement for  $V_{out}$  at different interval of  $V_{in}$  as well as the corresponding calculated  $V_{out}$  is shown in table 4.

$V_{in}$	$V_{out}(\text{measured})$	$V_{out}(\text{calculated})$	Difference (absolute value)
0.000 V	0.000 V	0.000 V	0.000 V
1.000 V	1.000 V	1.000 V	0.000 V
2.001 V	2.002 V	2.001 V	0.001 V
3.002 V	3.002 V	3.002 V	0.000 V
4.001 V	4.001 V	4.001 V	0.000 V
5.001 V	5.001 V	5.001 V	0.000 V

Table 4.  $V_{out}$  measured vs theoretically calculated for unity gain amplifier

- Based on the  $V_{out}$  measured at the 6 intervals of  $V_{in}$ , we plot  $V_{out}$  against  $V_{in}$  and obtain a graph as shown in figure 10. This is also the best-fit line.
- From figure 7, take two points **(0.50, 0.50)** and **(4.50, 4.50)** which is in range where the op-amp output is not saturated yet. The gradient of the plot in this unsaturated range is  $\frac{4.50-0.50}{4.50-0.50} = 1.00$ . **Thus, actual voltage gain of this non-inverting amplifier configuration = 1.00.**

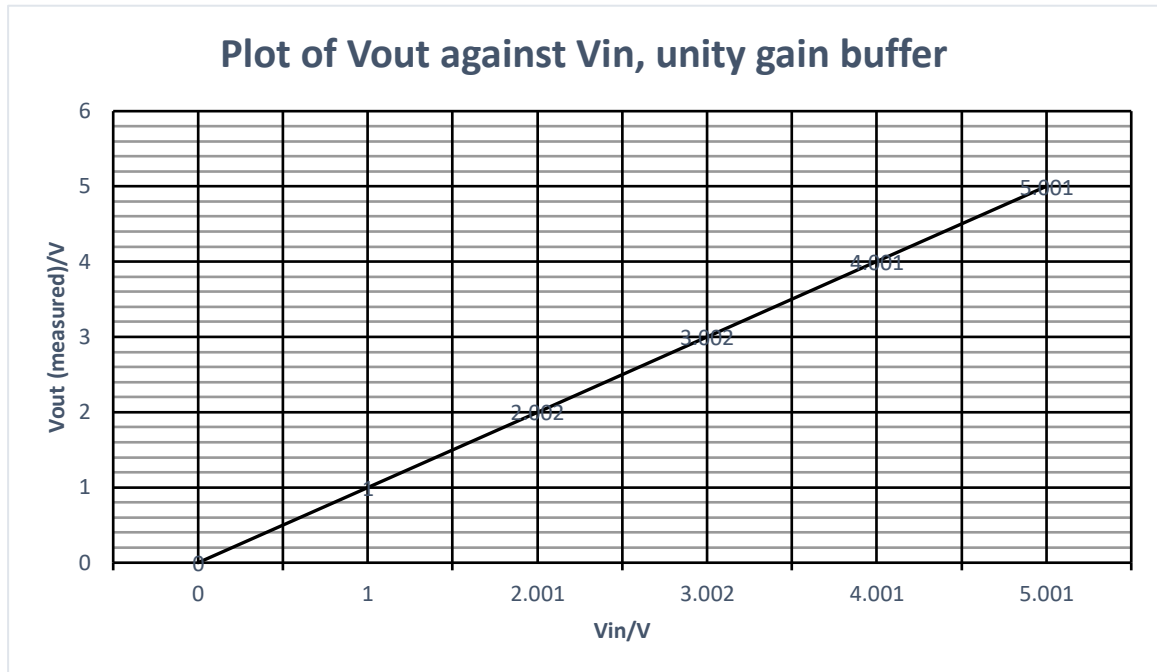


Figure 10 Plot of  $V_{out}$  against  $V_{in}$ , unity gain amp

#### Observations:

- **Actual voltage gain of unity amplifier is relatively close and consistent** with the theoretically predicted value and has **very high precision** (< 5.00% of error). Actual gain = 1.00 vs calculated gain = 1.00. Percentage error is 0%.
- The **voltage gain of unity gain amplifier is non-negative**, the output voltages' polarity is in phase with input voltages. This is as expected from the theoretical derived voltage gain since we are using the non-inverting amplifier to implement the unity gain buffer in this task, which is known to produce same output value with no change in polarity compared to input.
- **No saturation range in output** as max  $V_{out}$  recorded = 5.001V and is way lower than the saturated voltage level determined in part 2.1.a
- **The non-inverting amplifiers in our experiment behaves linearly** like expected. At every input interval, the output voltage is same as input. The gradient of the plot is a nice linear model, with very big linear region (no sharp swing of value of output voltage from 0 to saturated value).

#### b. Circuit Configuration with Sinusoidal Signal as Input

**Task 3: Connect  $V_{IN}$  to the output of a function generator. Connect the -ve terminal of the function generator to GND of the power supply (not to -15V). Set the function generator to supply a 1KHz sine wave of  $3V_{PK-PK}$  amplitude. Observe the waveforms at  $V_{IN}$  and  $V_{OUT}$  on the oscilloscope and sketch the waveforms.**

Following the procedure described above, make the change to figure 6 circuit configuration. We can obtain the waveform as shown in figure 11.

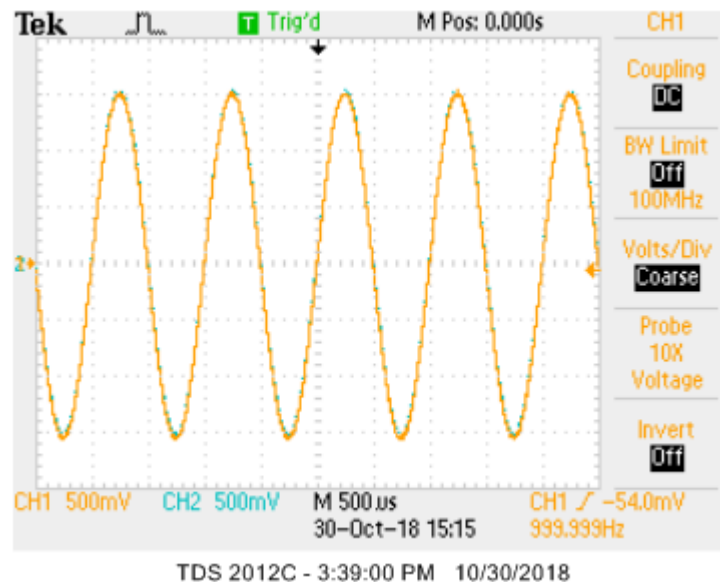


Figure 11 Waveform of  $V_{out}$  (blue) vs  $V_{in}$  (yellow) for unity gain amp

- **$V_{out}$  waveform obtained is a complete sinusoidal waveform.** This shown that there were no clipping phenomenon happens and the  $V_{out}$  due to  $V_{in}$  waveform was not at saturated value at all. This is as expected as the experimental gain was determined to be 1.00 for this amplifier and  $V_{in} = 3V$  (Peak-Peak from -1.5V to 1.5V, offset = 0 ). Thus the max  $V_{out} = 1.5V$  and min  $V_{out} = -1.5V$ , which is way lower than the saturated value of 12.936V and -12.936V determined above in 2.1.a.
- Polarity wise, **the  $V_{out}$  waveform is in phase with the  $V_{in}$  waveform.** This is the expected behaviour for a non-inverting amplifier and so is unity gain buffer with a positive gain.
- Amplitude wise, **the  $V_{out}$  waveform's amplitude is equal to the  $V_{in}$  amplitude** (consistently throughout the waveform such that we cannot see  $V_{out}$  as its waveform is hidden behind the waveform of  $V_{in}$ ). This is due to the unity gain thus  $V_{out} = V_{in}$  for whole waveform of  $V_{in}$ .
- The **waveform of input and output is continuous and  $V_{out}$  change linearly** with  $V_{in}$  value, shown by the corresponding sinusoidal waveform correspond to that of  $V_{in}$ .

### 3. Conclusions

In summary, **the 3 amplifiers** (inverting, non-inverting and unity gain amplifiers) being investigated in this experiment is **very close to ideal and behave consistently to what we have studied in class.**

**Non-inverting and unity gain amplifiers both have very high (close to infinity) input impedance** while this is not the case for inverting amplifiers (whose input impedance =  $R_1$ , shown in 2.1.a experiment). Thus, there will be a voltage loss from  $V_{\text{Supply}}$  going into the inverting terminal of this amplifier due to current drawn across  $R_1$ . This result in lower  $V_{\text{in}}$  received by the amplifier than the expected (should be = to  $V_s$ ) as discovered in the experiment.

**The saturated voltages value of the amplifiers in this experiment is capped at  $\pm 12.936\text{V}$  instead of  $\pm 15\text{V}$ .** This is due to the voltage decay happening in all non-ideal, practical amplifier, thus the max voltage output will always be about  $2.000\text{V}$  below the max voltage supply ( $\pm 15\text{V}$ ).

**All amplifiers** in this experiment **behaves linearly** as expected and has a very wide linear region, thus the problem of output voltage swinging from one saturated value to another with a very small change in  $V_{\text{in}}$  is not very significant (however, this is the case for inverting amplifiers for very high  $R_f$  value to  $R_1$  value ratio, illustrated in experiment 2.1). This is shown when we investigate the behaviour of all amplifiers' output when the input is a sinusoidal waveform. In these cases, none of the amplifiers have clipping behaviour waveform (as long as reasonable level of input used).

**Different amplifiers with different gain value** ( $\geq 0$  for non-inverting amplifiers (including unity gain) and  $< 0$  for inverting amplifiers) **can be combined to form more complex circuit of different purposes** (depend on application requirements). In these cases, the loading effect is minimal.